

Mihir Phadke (015745301)

Jai Nayyar (015176655)

Ryan Smith (015792504)

Thurman Dao (015708589)

Haydon Behl

Anson Lee

Lab 3

Mar 6, 2025

1.) CPU module Design Code

```
`timescale 1ns / 1ps

module cpu(
    input rst_n,
    input clk,
    output reg [31:0] imem_addr,
    input [31:0] imem_insn,
    output reg [31:0] dmem_addr,
    inout [31:0] dmem_data,
    output reg dmem_wen
);
    // stall register
    reg stall;
    // IF/ID pipeline register
    reg [31:0] IF_ID_insn, IF_ID_pc;
    // ID/EX pipeline register
    reg [31:0] ID_EX_pc, ID_EX_imm;
    reg [4:0] ID_EX_dest, ID_EX_src1;
    reg [2:0] ID_EX_alu_ctrl;
    // EX/MEM pipeline register
    reg [31:0] EX_MEM_alu_result;
    reg [4:0] EX_MEM_dest;
    // MEM/WB pipeline registers
    reg signed [31:0] MEM_WB_result;
    reg [4:0] MEM_WB_dest;
    reg MEM_WB_wen;

    // Clock Cycle Counter
    reg [15:0] cycle_counter;

    always @(posedge clk or negedge rst_n) begin
```

```

        if (!rst_n)
            cycle_counter <= 16'b0;
        else
            cycle_counter <= cycle_counter + 1;
    end

    // Program Counter Module
    wire [31:0] pc, next_pc;

    PC pc_module(
        .rst_n(rst_n),
        .clk(clk),
        .stall(stall),
        .next_pc(next_pc),
        .pc(pc)
    );

    assign next_pc = pc + 4;
    assign imem_addr = pc;

    // Instruction Fetch Stage
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            IF_ID_insn <= 32'b0;
            IF_ID_pc <= 32'b0;
        end else if (stall != 1'b1) begin
            IF_ID_insn <= imem_insn;
            IF_ID_pc <= pc;
        end
    end

    // Decode Stage
    wire [6:0] opcode;
    wire [4:0] destination_reg, source_reg1;
    wire [2:0] funct3;
    wire [11:0] imm;

    instruction_decoder decoder(
        .imem_insn(IF_ID_insn),
        .opcode(opcode),
        .destination_reg(destination_reg),
        .funct3(funct3),
        .source_reg1(source_reg1),

```

```

        .imm(imm)
    );

    // Hazard detection
    always @(*) begin
        // Check if source register of current instruction matches
        // destination register in pipeline
        if ((ID_EX_dest != 5'b0) && (ID_EX_dest == source_reg1)) begin
            stall = 1'b1;
        end else if ((EX_MEM_dest != 5'b0) && (EX_MEM_dest == source_reg1))
begin
            stall = 1'b1;
        end else if ((MEM_WB_dest != 5'b0) && (MEM_WB_dest == source_reg1))
begin
            stall = 1'b1;
        end else begin
            stall = 1'b0;
        end
    end
end

// ALU Control
wire [2:0] alu_ctrl_temp;

ALUDecoder alu_decoder(
    .opcode(opcode),
    .funct3(funct3),
    .alu_ctrl(alu_ctrl_temp)
);

always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        ID_EX_pc <= 32'b0;
        ID_EX_dest <= 5'b0;
        ID_EX_src1 <= 5'b0;
        ID_EX_imm <= 32'b0;
        ID_EX_alu_ctrl <= 3'b111;
    end else begin
        ID_EX_pc <= IF_ID_pc;
        ID_EX_dest <= destination_reg;
        ID_EX_src1 <= source_reg1;
        ID_EX_imm <= {{20{imm[11]}}, imm};
        ID_EX_alu_ctrl <= alu_ctrl_temp;
    end
end

```

```

end

// Register File
wire [31:0] reg_data1;

register_file reg_file(
    .clk(clk),
    .rst_n(rst_n),
    .wen(MEM_WB_wen),
    .destination_reg(MEM_WB_dest),
    .source_reg1(ID_EX_src1),
    .write_data(MEM_WB_result),
    .read_data1(reg_data1)
);

// Execute Stage
wire [31:0] alu_result;

ALU alu(
    .op1(reg_data1),
    .op2(ID_EX_imm),
    .alu_ctrl(ID_EX_alu_ctrl),
    .result(alu_result)
);

always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        EX_MEM_alu_result <= 32'b0;
        EX_MEM_dest <= 5'b0;
    end else begin
        EX_MEM_alu_result <= alu_result;
        EX_MEM_dest <= ID_EX_dest;
    end
end

always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        MEM_WB_result <= 32'b0;
        MEM_WB_dest <= 5'b0;
        MEM_WB_wen <= 1'b0;
    end else begin
        MEM_WB_result <= EX_MEM_alu_result;
        MEM_WB_dest <= EX_MEM_dest;
    end
end

```

```

        MEM_WB_wen <= (EX_MEM_dest != 5'b0);
    end
end

// open files
integer fd_pc, fd_data;
initial begin
    fd_pc = $fopen("pc.txt", "w");
    fd_data = $fopen("data.txt", "w");
    if (fd_pc == 0 || fd_data == 0) begin
        $display("Error: Could not open file.");
        $finish;
    end
    $display("File descriptors: fd_pc = %0d, fd_data = %0d", fd_pc,
fd_data);
end

// print to trace files
always @(posedge clk or negedge rst_n) begin
    if(!rst_n) begin

    end else begin
        $display("IF_ID_pc: %h, MEM_WB_result: %h, MEM_WB_dest: %h",
IF_ID_pc, MEM_WB_result, MEM_WB_dest);
        $fdisplay(fd_pc, "PC: 0x%h", IF_ID_pc);
        $fdisplay(fd_data, "MEM_WB_result: %d", MEM_WB_result);
        $fdisplay(fd_data, "MEM_WB_dest: %d", MEM_WB_dest);
        $fdisplay(fd_data, "-----");
    end
end

// close files
initial begin
    #1000
    $fclose(fd_pc);
    $fclose(fd_data);
    $display("Files closed successfully.");
end
endmodule

// Program Counter Module
module PC(

```

```

    input rst_n,
    input clk,
    input stall,
    input [31:0] next_pc,
    output reg [31:0] pc
);
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n)
            pc <= 32'b0;
        else if (!stall)
            pc <= next_pc;
        end
    endmodule

```

// Instruction Decoder Module

```

module instruction_decoder(
    input [31:0] imem_insn,
    output reg [6:0] opcode,
    output reg [4:0] destination_reg,
    output reg [2:0] funct3,
    output reg [4:0] source_reg1,
    output reg [11:0] imm
);
    always @(*) begin
        opcode = imem_insn[6:0];
        destination_reg = imem_insn[11:7];
        funct3 = imem_insn[14:12];
        source_reg1 = imem_insn[19:15];
        imm = imem_insn[31:20];
    end
endmodule

```

// ALU Decoder Module

```

module ALUDecoder(
    input [6:0] opcode,
    input [2:0] funct3,
    output reg [2:0] alu_ctrl
);
    always @(*) begin
        case (opcode)
            7'b0010011: begin

```

```

        case (funct3)
            3'b000: alu_ctrl = 3'b000; // ADDI
            default: alu_ctrl = 3'b111;
        endcase
    end
    default: alu_ctrl = 3'b111;
endcase
end
endmodule

```

// ALU Module

```

module ALU(
    input [31:0] op1,
    input [31:0] op2,
    input [2:0] alu_ctrl,
    output reg [31:0] result
);
    always @(*) begin
        case (alu_ctrl)
            3'b000: result = op1 + op2; // ADDI
            default: result = 32'b0;
        endcase
    end
endmodule

```

// Register File Module

```

module register_file(
    input clk,
    input rst_n,
    input wen,
    input [4:0] destination_reg,
    input [4:0] source_reg1,
    input [31:0] write_data,
    output reg [31:0] read_data1
);
    reg [31:0] registers [0:31];

    initial begin
        integer i;
        for (i = 0; i < 32; i = i + 1)
            registers[i] = 32'b0;
    end
endmodule

```

```

end

always @(*) begin
    read_data1 = registers[source_reg1];
end

always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        integer i;
        for (i = 0; i < 32; i = i + 1)
            registers[i] <= 32'b0;
    end else if (wen && (destination_reg != 5'b0)) begin
        registers[destination_reg] <= write_data;
    end
end

end
endmodule

```

2.) The Two Trace Files (Screenshots within the files or attached when turned in)

Non-hazard trace files:

```

12 -----
13 MEM_WB_result:          5
14 MEM_WB_dest:  5
15 -----
16 MEM_WB_result:        -10
17 MEM_WB_dest:  6
18 -----
19 MEM_WB_result:          3
20 MEM_WB_dest:  7
21 -----
22 MEM_WB_result:         -1
23 MEM_WB_dest: 28
24 -----
25 MEM_WB_result:          5
26 MEM_WB_dest: 29
27 -----
28 MEM_WB_result:         11
29 MEM_WB_dest: 30
30 -----
31 MEM_WB_result:         -6
32 MEM_WB_dest: 31
33 -----

```


The image above shows the trace files for the result written back to the register and the destination register for the non-hazards simulation.

| | |
|----|----------------|
| 1 | PC: 0x00000000 |
| 2 | PC: 0x00000000 |
| 3 | PC: 0x00000004 |
| 4 | PC: 0x00000008 |
| 5 | PC: 0x0000000c |
| 6 | PC: 0x00000010 |
| 7 | PC: 0x00000014 |
| 8 | PC: 0x00000018 |
| 9 | PC: 0x0000001c |
| 10 | PC: 0x00000020 |
| 11 | PC: 0x00000024 |
| 12 | PC: 0x00000028 |
| 13 | PC: 0x0000002c |
| 14 | PC: 0x00000030 |
| 15 | PC: 0x00000034 |
| 16 | PC: 0x00000038 |
| 17 | PC: 0x0000003c |
| 18 | PC: 0x00000040 |
| 19 | PC: 0x00000044 |
| 20 | PC: 0x00000048 |
| 21 | PC: 0x0000004c |
| 22 | PC: 0x00000050 |
| 23 | PC: 0x00000054 |
| 24 | PC: 0x00000058 |
| 25 | PC: 0x0000005c |
| 26 | PC: 0x00000060 |
| 27 | PC: 0x00000064 |
| 28 | PC: 0x00000068 |
| 29 | PC: 0x0000006c |
| 30 | PC: 0x00000070 |
| 31 | PC: 0x00000074 |
| 32 | PC: 0x00000078 |
| 33 | PC: 0x0000007c |
| 34 | PC: 0x00000080 |
| 35 | PC: 0x00000084 |
| 36 | PC: 0x00000088 |
| 37 | PC: 0x0000008c |
| 38 | PC: 0x00000090 |
| 39 | PC: 0x00000094 |
| 40 | PC: 0x00000098 |

The image above shows the program counter for the non-hazards simulation.

Hazard trace files:

| | |
|----|----------------|
| 1 | PC: 0x00000000 |
| 2 | PC: 0x00000000 |
| 3 | PC: 0x00000004 |
| 4 | PC: 0x00000004 |
| 5 | PC: 0x00000004 |
| 6 | PC: 0x00000004 |
| 7 | PC: 0x00000008 |
| 8 | PC: 0x0000000c |
| 9 | PC: 0x00000010 |
| 10 | PC: 0x00000010 |
| 11 | PC: 0x00000014 |
| 12 | PC: 0x00000014 |
| 13 | PC: 0x00000018 |
| 14 | PC: 0x00000018 |
| 15 | PC: 0x00000018 |
| 16 | PC: 0x00000018 |
| 17 | PC: 0x0000001c |
| 18 | PC: 0x00000020 |
| 19 | PC: 0x00000024 |
| 20 | PC: 0x00000028 |
| 21 | PC: 0x0000002c |
| 22 | PC: 0x00000030 |
| 23 | PC: 0x00000034 |
| 24 | PC: 0x00000038 |
| 25 | PC: 0x0000003c |
| 26 | PC: 0x00000040 |
| 27 | PC: 0x00000044 |
| 28 | PC: 0x00000048 |
| 29 | PC: 0x0000004c |
| 30 | PC: 0x00000050 |
| 31 | PC: 0x00000054 |
| 32 | PC: 0x00000058 |
| 33 | PC: 0x0000005c |
| 34 | PC: 0x00000060 |
| 35 | PC: 0x00000064 |
| 36 | PC: 0x00000068 |
| 37 | PC: 0x0000006c |
| 38 | PC: 0x00000070 |
| 39 | PC: 0x00000074 |
| 40 | PC: 0x00000078 |
| 41 | PC: 0x0000007c |
| 42 | PC: 0x00000080 |
| 43 | PC: 0x00000084 |
| 44 | PC: 0x00000088 |
| 45 | PC: 0x0000008c |
| 46 | PC: 0x00000090 |
| 47 | PC: 0x00000094 |
| 48 | PC: 0x00000098 |

The image above shows the program counter for the hazards simulation.

```

12 -----
13 MEM_WB_result:      5
14 MEM_WB_dest:  5
15 -----
16 MEM_WB_result:     -10
17 MEM_WB_dest:  6
18 -----
19 MEM_WB_result:     -10
20 MEM_WB_dest:  6
21 -----
22 MEM_WB_result:      -5
23 MEM_WB_dest:  6
24 -----
25 MEM_WB_result:      -5
26 MEM_WB_dest:  6
27 -----
28 MEM_WB_result:       8
29 MEM_WB_dest:  7
30 -----
31 MEM_WB_result:       4
32 MEM_WB_dest: 28
33 -----
34 MEM_WB_result:       0
35 MEM_WB_dest: 29
36 -----
37 MEM_WB_result:       0
38 MEM_WB_dest: 29
39 -----
40 MEM_WB_result:      15
41 MEM_WB_dest: 30
42 -----
43 MEM_WB_result:      15
44 MEM_WB_dest: 30
45 -----
46 MEM_WB_result:     -11
47 MEM_WB_dest: 31
48 -----
49 MEM_WB_result:       4
50 MEM_WB_dest: 31
51 -----
52 MEM_WB_result:       4
53 MEM_WB_dest: 31
54 -----
55 MEM_WB_result:       4
56 MEM_WB_dest: 31
57 -----


```

The image above shows the trace file for the result written back to the register and which register it was written to for the hazards simulation.

3.) Post Simulation Convergence with results matching the same results for both hazard and non hazard

Non-hazard waveforms:


| Registers | Floating Point | Control and Status |
|-----------|----------------|--------------------|
| Name | Number | Value |
| zero | 0 | 0 |
| ra | 1 | 0 |
| sp | 2 | 2147479548 |
| gp | 3 | 268468224 |
| tp | 4 | 0 |
| t0 | 5 | 5 |
| t1 | 6 | -10 |
| t2 | 7 | 3 |
| s0 | 8 | 0 |
| s1 | 9 | 0 |
| a0 | 10 | 0 |
| a1 | 11 | 0 |
| a2 | 12 | 0 |
| a3 | 13 | 0 |
| a4 | 14 | 0 |
| a5 | 15 | 0 |
| a6 | 16 | 0 |
| a7 | 17 | 0 |
| s2 | 18 | 0 |
| s3 | 19 | 0 |
| s4 | 20 | 0 |
| s5 | 21 | 0 |
| s6 | 22 | 0 |
| s7 | 23 | 0 |
| s8 | 24 | 0 |
| s9 | 25 | 0 |
| s10 | 26 | 0 |
| s11 | 27 | 0 |
| t3 | 28 | -1 |
| t4 | 29 | 5 |
| t5 | 30 | 11 |
| t6 | 31 | -6 |
| pc | | 4194336 |

 

The waveforms above show the values from the no hazards test. As we can see the values match the values in the rars simulation for no hazards.

Hazard waveforms:

| Registers | Floating Point | Control and Status |
|-----------|----------------|--------------------|
| Name | Number | Value |
| zero | 0 | 0 |
| ra | 1 | 0 |
| sp | 2 | 2147479548 |
| gp | 3 | 268468224 |
| tp | 4 | 0 |
| t0 | 5 | 5 |
| t1 | 6 | -5 |
| t2 | 7 | 8 |
| s0 | 8 | 0 |
| s1 | 9 | 0 |
| a0 | 10 | 0 |
| a1 | 11 | 0 |
| a2 | 12 | 0 |
| a3 | 13 | 0 |
| a4 | 14 | 0 |
| a5 | 15 | 0 |
| a6 | 16 | 0 |
| a7 | 17 | 0 |
| s2 | 18 | 0 |
| s3 | 19 | 0 |
| s4 | 20 | 0 |
| s5 | 21 | 0 |
| s6 | 22 | 0 |
| s7 | 23 | 0 |
| s8 | 24 | 0 |
| s9 | 25 | 0 |
| s10 | 26 | 0 |
| s11 | 27 | 0 |
| t3 | 28 | 4 |
| t4 | 29 | 0 |
| t5 | 30 | 15 |
| t6 | 31 | 4 |
| pc | | 4194336 |

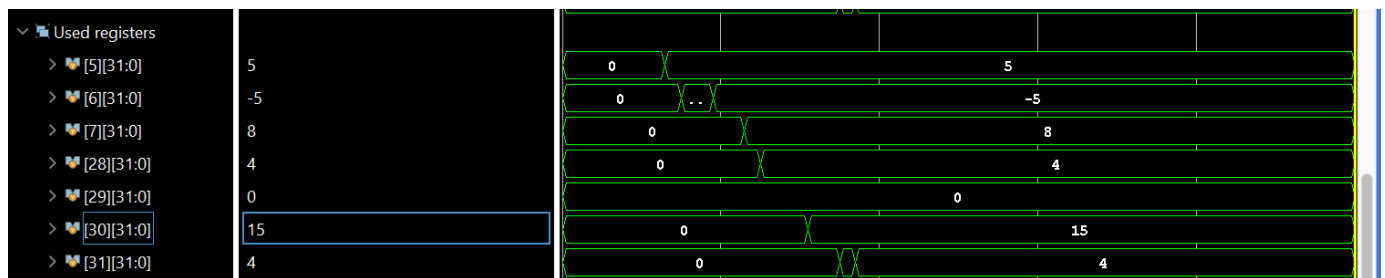

The image above shows the waveform from the hazards test. As we can see the values in the registers match the rars simulation shown above for hazards.

Conclusion/ Lab Learning:

In this lab, we learned how to implement a pipelined RISC-V processor. One of the things that we had planned out was dividing the pipeline stages and understanding how the RISC-V assembly code operates which includes the PC and CPU structure via the gateways to the various modules handling the

data down the pipeline. Understanding how the processor deciphers assembly code into binary code and does calculations was instrumental to understanding and scripting this processor. In this particular lab, we implemented the basic instruction execution “addi” and coded how the instructions are handled, which included how the binary is formatted in I format. Another obstacle in this lab was the hazard handling, as the instruction had to navigate the pipeline using stalls to handle the hazard, which we had to verify using `addi_nohazard.dat` and `addi_hazard.dat` respectively.