

Mihir Phadke  
Haydon Behl  
Ryan Smith  
Jai Nayyar  
Thurman Dao  
Anson Lee  
Apr 16, 2025

```
module ALU(
    input [31:0] op1,
    input [31:0] op2,
    input [2:0] funct3,
    input [6:0] funct7,
    input [4:0] shamt,
    input [2:0] insn_type,
    output reg [31:0] result
);
always @ (*) begin
    case (insn_type)
        // I-type arithmetic instructions
        3'b000: begin
            case (funct3)
                3'b000: result = op1 + op2; // ADDI
                3'b010: result = ($signed(op1) < $signed(op2)) ? 1 : 0;
                // SLTI
                3'b011: result = (op1 < op2) ? 1 : 0; // SLTIU
                3'b100: result = op1 ^ op2; // XORI
                3'b110: result = op1 | op2; // ORI
                3'b111: result = op1 & op2; // ANDI
                3'b001: result = op1 << shamt; // SLLI
                3'b101: begin
                    if (funct7 == 7'b0100000)
                        result = $signed(op1) >>> shamt; // SRAI
                    else if (funct7 == 7'b0000000)
                        result = op1 >> shamt; // SRLI
                    else
                        result = 32'b0;
                end
            end
            default: result = 32'b0;
        endcase
    end
    // R-type arithmetic instructions
    3'b001: begin
```

```

        case(func3)
            3'b000: begin
                if(func7 == 7'b0000000)
                    result = op1 + op2; // ADD
                else if(func7 == 7'b0100000)
                    result = op1 - op2; // SUB
                end
            3'b001: result = op1 << op2[4:0]; // SLL
            3'b010: result = ($signed(op1) < $signed(op2)) ? 1 : 0;
// SLT

            3'b011: result = (op1 < op2) ? 1 : 0; // SLTU
            3'b100: result = op1 ^ op2; // XOR
            3'b101: begin
                if(func7 == 7'b0100000)
                    result = $signed(op1) >>> op2[4:0]; // SRA
                else if(func7 == 7'b0000000)
                    result = op1 >> op2[4:0]; // SRL
                end
            3'b110: result = op1 | op2; // OR
            3'b111: result = op1 & op2; // AND
            default: result = 32'b0;
        endcase
    end
    // S-type (store) and Load: effective address = base + offset.
    3'b010, 3'b011: begin
        result = op1 + op2;
    end
    // U-type
    3'b100: begin
        result = op1 + op2;
    end
    // J-type (jump): target address = base + offset.
    3'b101: begin
        result = op1 + op2;
    end
    // B-type (branch): target address = PC + offset.
    3'b110: begin
        result = op1 + op2;
    end
    // Default: result = 0.
    default: result = 32'b0;
endcase
end

```

```
endmodule
```

```
module PC(
    input      rst_n,
    input      clk,
    input      stall,
    input      branch_jump,    // Asserted when a branch or jump is taken
    input [31:0] new_pc,       // Target address when branch/jump is
    active
    output reg [31:0] pc
);
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n)
            pc <= 32'b0;
        else if (stall)
            pc <= pc;           // Hold PC during a stall
        else if (branch_jump)
            pc <= new_pc;       // Load new target address for branch/jump
        else
            pc <= pc + 4;       // Otherwise, proceed sequentially
    end
endmodule
```

```
module cpu(
    input      rst_n,
    input      clk,
    output [31:0] imem_addr,
    input [31:0] imem_insn,
    output reg [31:0] dmem_addr,
    inout [31:0] dmem_data,
    output reg      dmem_wen,
    output [3:0] byte_en
);
    // Stall signal (for hazards)
    reg stall;

    //-----
    // Pipeline Registers
    //-----
    // IF/ID pipeline registers
    reg [31:0] IF_ID_insn, IF_ID_pc;
```

```

reg ID_wen;
reg ID_dmem_wen;
// A flush register to clear IF/ID on branch/jump.
reg flush_pipeline;

// ID/EX pipeline registers
reg [31:0] ID_EX_pc, ID_EX_imm;
reg [4:0] ID_EX_dest, ID_EX_src1, ID_EX_src2;
reg [2:0] ID_EX_insn_type;
reg [2:0] ID_EX_funct3;
reg [4:0] ID_EX_shamt;
reg [6:0] ID_EX_funct7;
reg ID_EX_alu_op_mux;
reg ID_EX_wen;
reg ID_EX_dmem_wen;
reg [31:0] ID_EX_store_data;

// EX/MEM pipeline registers
reg [31:0] EX_MEM_alu_result;
reg [4:0] EX_MEM_dest;
reg EX_MEM_wen;
reg EX_MEM_dmem_wen;
reg [2:0] EX_MEM_insn_type; // (e.g. 010: store, 011: Load)
reg [2:0] EX_MEM_funct3;
reg [31:0] EX_MEM_store_data;

// MEM/WB pipeline registers
reg signed [31:0] MEM_WB_result;
reg [4:0] MEM_WB_dest;
reg MEM_WB_wen;
reg [2:0] MEM_WB_insn_type;
reg [2:0] MEM_WB_funct3;
reg [31:0] MEM_WB_alu_result;
reg [31:0] MEM_WB_ram_result;

//-----
// dmem_data Tri-state Control & Byte Enable Signals
//-----
reg [31:0] dmem_data_out;
assign dmem_data = (dmem_wen) ? dmem_data_out : 32'hz;

reg [3:0] byte_en_dmem_reg;
assign byte_en = byte_en_dmem_reg;

```

```

reg [3:0] byte_en_reg; // For register file (if needed)

//-----
// Cycle Counter (for debugging/tracing)
//-----
reg [15:0] cycle_counter;
always @(posedge clk or negedge rst_n) begin
    if (!rst_n)
        cycle_counter <= 16'b0;
    else
        cycle_counter <= cycle_counter + 1;
end

//-----
// Program Counter (PC) Module Instantiation
// The PC now accepts branch/jump override signals.
//-----
wire [31:0] pc;
wire branch_jump;
wire [31:0] new_pc;

PC pc_module(
    .rst_n(rst_n),
    .clk(clk),
    .stall(stall),
    .branch_jump(branch_jump),
    .new_pc(branch_target),
    .pc(pc)
);

// The instruction memory address is driven by the PC.
assign imem_addr = pc;

//-----
// Flush Pipeline Register
// We register the branch/jump decision (from EX stage) so that the
IF/ID
// registers are flushed in the next clock cycle.
//-----
always @(posedge clk or negedge rst_n) begin
    if ((!rst_n) | flush_pipeline)
        flush_pipeline <= 1'b0;
    else

```

```

        flush_pipeline <= branch_jump;
    end

    //-----
    // Instruction Fetch (IF) Stage
    //-----
    always @(posedge clk or negedge rst_n) begin
        if ((!rst_n) | branch_taken) begin // Do not grab next insn if we
            are about to jump!
                IF_ID_insn <= 32'b0;
                IF_ID_pc   <= 32'b0;
            end else begin
                IF_ID_insn <= imem_insn;
                IF_ID_pc   <= pc;
            end
        end
    end

    //-----
    // Decode Stage: Instruction Decoder Instantiation
    //-----
    // Our updated decoder outputs a 32-bit immediate.
    wire [4:0] destination_reg;
    wire [2:0] funct3;
    wire [4:0] source_reg1;
    wire [4:0] source_reg2;
    wire [31:0] imm;
    wire [6:0] funct7;
    wire [4:0] shamt;
    wire [2:0] insn_type;
    // insn_type encoding:
    // 000: I-type, 001: R-type, 010: S-type, 011: Load,
    // 100: U-type, 101: J-type, 110: Branch, 111: Default (NOP)
    wire alu_op_mux;

    instruction_decoder decoder (
        .imem_insn(IF_ID_insn),
        .destination_reg(destination_reg),
        .funct3(funct3),
        .source_reg1(source_reg1),
        .source_reg2(source_reg2),
        .imm(imm),
        .funct7(funct7),
        .shamt(shamt),

```

```

        .insn_type(insn_type),
        .alu_op_mux(alu_op_mux),
        .wen(ID_wen),
        .dmem_wen(ID_dmem_wen)
    );

    //-----
    // ID/EX Pipeline Register Update
    //-----
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n | branch_jump) begin
            ID_EX_pc          <= 32'b0;
            ID_EX_dest        <= 5'b0;
            ID_EX_src1        <= 5'b0;
            ID_EX_src2        <= 5'b0;
            ID_EX_imm         <= 32'b0;
            ID_EX_func3       <= 3'b0;
            ID_EX_func7       <= 7'b0;
            ID_EX_insn_type   <= 3'b111; // Default to NOP
            ID_EX_shamt       <= 5'b0;
            ID_EX_alu_op_mux  <= 1'b0;
            ID_EX_wen         <= 1'b0;
            ID_EX_dmem_wen    <= 1'b0;
            ID_EX_store_data  <= 32'b0;
        end else begin
            ID_EX_pc          <= IF_ID_pc;
            ID_EX_dest        <= destination_reg;
            ID_EX_src1        <= source_reg1;
            ID_EX_src2        <= source_reg2;
            ID_EX_insn_type   <= insn_type;
            ID_EX_func3       <= funct3;
            ID_EX_func7       <= funct7;
            ID_EX_shamt       <= shamt;
            ID_EX_alu_op_mux  <= alu_op_mux;
            ID_EX_imm         <= imm;
            ID_EX_wen         <= ID_wen;
            ID_EX_dmem_wen    <= ID_dmem_wen;
        end
    end

    //-----
    // Register File Instance
    //-----

```

```

wire [31:0] reg_data1;
wire [31:0] reg_data2;
register_file reg_file (
    .clk(clk),
    .rst_n(rst_n),
    .wen(MEM_WB_wen),
    .destination_reg(MEM_WB_dest),
    .source_reg1(ID_EX_src1),
    .source_reg2(ID_EX_src2),
    .write_data(MEM_WB_result),
    .byte_en(byte_en_reg),
    .read_data1(reg_data1),
    .read_data2(reg_data2)
);

//-----
//Forwarding Logic (for ALU operands)
//-----
wire [31:0] forwarded_op1;
wire [31:0] forwarded_op2;

// Register "skips" for when the requested data is not yet written to
reg.
assign forwarded_op1 = ((EX_MEM_dest != 5'b0) && (EX_MEM_dest ==
ID_EX_src1) && EX_MEM_wen) ? EX_MEM_alu_result :
    ((MEM_WB_dest != 5'b0) && (MEM_WB_dest ==
ID_EX_src1) && MEM_WB_wen) ? MEM_WB_result :
    reg_data1;
assign forwarded_op2 = (ID_EX_alu_op_mux) ? ID_EX_imm :
    ((EX_MEM_dest != 5'b0) && (EX_MEM_dest ==
ID_EX_src2) && EX_MEM_wen) ? EX_MEM_alu_result :
    ((MEM_WB_dest != 5'b0) && (MEM_WB_dest ==
ID_EX_src2) && MEM_WB_wen) ? MEM_WB_result :
    reg_data2;

//-----
// ALU Operand for Jump Instructions
// For JAL, the base should be the PC. For JALR, use register.
//-----
wire [31:0] alu_op1;
assign alu_op1 = ((ID_EX_insn_type == 3'b101) && (ID_EX_src1 == 5'b0))
? ID_EX_pc : forwarded_op1;

```



```

//-----
// Execute (EX) Stage: ALU Instance
//-----
wire [31:0] alu_result;
ALU alu (
    .op1(alu_op1),
    .op2(forwarded_op2),
    .shamt(ID_EX_shamt),
    .funct3(ID_EX_funct3),
    .funct7(ID_EX_funct7),
    .insn_type(ID_EX_insn_type),
    .result(alu_result)
);

//-----
// Branch Decision & Target Computation (EX Stage)
//-----
wire branch_taken;
wire [31:0] branch_target;

assign branch_taken = (flush_pipeline) ? 1'b0 : // cant jump during a
flush
    (ID_EX_insn_type == 3'b101) ? 1'b1 : // JAL
    (ID_EX_insn_type == 3'b110) ?
    ((ID_EX_funct3 == 3'b000) ? (forwarded_op1 == forwarded_op2) : //
BEQ
    (ID_EX_funct3 == 3'b001) ? (forwarded_op1 != forwarded_op2) : //
BNE
    (ID_EX_funct3 == 3'b100) ? ($signed(forwarded_op1) <
$signed(forwarded_op2)) : // BLT
    (ID_EX_funct3 == 3'b101) ? ($signed(forwarded_op1) >=
$signed(forwarded_op2)) : // BGE
    (ID_EX_funct3 == 3'b110) ? (forwarded_op1 < forwarded_op2) : //
BLTU
    (ID_EX_funct3 == 3'b111) ? (forwarded_op1 >= forwarded_op2) : //
BGEU
    1'b0)
    : 1'b0;

assign branch_target = ID_EX_pc + ID_EX_imm;

//-----
// Branch/Jump Control Signals for PC Update

```

```

// For jumps (insn_type 3'b101) the branch is unconditional.
// For branches (insn_type 3'b110) use branch_taken.
//-----
assign branch_jump = (((ID_EX_insn_type == 3'b101) || ((ID_EX_insn_type
== 3'b110) && branch_taken)) && (!flush_pipeline));

//-----
// EX/MEM Pipeline Register Update
//-----
always @(posedge clk or negedge rst_n) begin
    if ((!rst_n) | branch_jump) begin
        EX_MEM_alu_result <= 32'b0;
        EX_MEM_dest      <= 5'b0;
        EX_MEM_wen       <= 1'b0;
        EX_MEM_dmem_wen  <= 1'b0;
        EX_MEM_func3     <= 3'b0;
        EX_MEM_insn_type <= 3'b0;
        EX_MEM_store_data <= 32'b0;
    end else begin
        EX_MEM_alu_result <= alu_result;
        EX_MEM_dest      <= ID_EX_dest;
        EX_MEM_wen       <= ID_EX_wen;
        EX_MEM_dmem_wen  <= ID_EX_dmem_wen;
        EX_MEM_func3     <= ID_EX_func3;
        EX_MEM_insn_type <= ID_EX_insn_type;
        EX_MEM_store_data <= ID_EX_store_data;
    end
end

//-----
// Memory (MEM) Stage
//-----
// Fix X values on dmem_data.
wire [31:0] fixed_data;
genvar i;
generate
    for(i = 0; i < 32; i = i + 1) begin : fix_x_bits
        assign fixed_data[i] = (dmem_data[i] === 1'bx) ? 1'b1 :
dmem_data[i];
    end
endgenerate

// Load extraction logic (active for load instructions, insn_type

```

```

3'b011)
    wire [31:0] load_result;
    assign load_result = (MEM_WB_insn_type == 3'b011) ? (
        (MEM_WB_funct3 == 3'b000) ? { {24{fixed_data[7]}},
fixed_data[7:0]} : // LB
        (MEM_WB_funct3 == 3'b001) ? { {16{fixed_data[15]}},
fixed_data[15:0]} : // LH
        (MEM_WB_funct3 == 3'b010) ? fixed_data :
// LW
        (MEM_WB_funct3 == 3'b100) ? {24'b0, fixed_data[7:0]} :
// LBU
        (MEM_WB_funct3 == 3'b101) ? {16'b0, fixed_data[15:0]} :
// LHU
        fixed_data
    ) : 32'b0;

    // Write-back selection: use load_result for loads; otherwise use the
ALU result.
    assign MEM_WB_result = (MEM_WB_insn_type == 3'b011) ? load_result :
MEM_WB_alu_result;

    //-----
// MEM/WB Pipeline Register Update
//-----
    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            MEM_WB_alu_result <= 32'b0;
            MEM_WB_dest      <= 5'b0;
            MEM_WB_wen       <= 1'b0;
            MEM_WB_insn_type<= 3'b0;
            MEM_WB_funct3    <= 3'b0;
            dmem_wen         <= 1'b0;
            dmem_addr        <= 32'b0;
            byte_en_dmem_reg<= 4'b0;
            byte_en_reg      <= 4'b0;
        end else begin
            dmem_data_out = EX_MEM_store_data;
            if (EX_MEM_insn_type == 3'b011) begin
                dmem_addr <= EX_MEM_alu_result; // Effective address for
Load

                byte_en_dmem_reg <= 4'b0000;
                byte_en_reg <= 4'b1111;
            end else if (EX_MEM_insn_type == 3'b010) begin

```

```

        dmem_addr <= EX_MEM_alu_result; // Effective address for
store

        case (EX_MEM_func3)
            3'b000: byte_en_dmem_reg <= 4'b0001; // SB
            3'b001: byte_en_dmem_reg <= 4'b0011; // SH
            3'b010: byte_en_dmem_reg <= 4'b1111; // SW
            default: byte_en_dmem_reg <= 4'b0000;
        endcase
        byte_en_reg <= 4'b0000;
    end else begin
        dmem_addr <= 32'b0;
        byte_en_dmem_reg <= 4'b0000;
        byte_en_reg <= 4'b1111;
    end

    MEM_WB_func3      <= EX_MEM_func3;
    MEM_WB_alu_result <= EX_MEM_alu_result;
    MEM_WB_dest       <= EX_MEM_dest;
    MEM_WB_wen        <= EX_MEM_wen;
    MEM_WB_insn_type  <= EX_MEM_insn_type;
    dmem_wen          <= EX_MEM_dmem_wen;
end
end

//-----
// File Trace Output (for debugging/tracing)
//-----
integer fd_pc, fd_data;
initial begin
    fd_pc = $fopen("pc.txt", "w");
    fd_data = $fopen("data.txt", "w");
    if (fd_pc == 0 || fd_data == 0) begin
        $display("Error: Could not open file.");
        $finish;
    end
end

always @(posedge clk or negedge rst_n) begin
    if (rst_n) begin
        $display("IF_ID_pc: %h, MEM_WB_result: %h, MEM_WB_dest: %h",
IF_ID_pc, MEM_WB_result, MEM_WB_dest);
        $fdisplay(fd_pc, "PC: 0x%h", IF_ID_pc);
        $fdisplay(fd_data, "MEM_WB_result: %d", MEM_WB_result);
    end
end

```

```

        $fdisplay(fd_data, "MEM_WB_dest: %d", MEM_WB_dest);
        $fdisplay(fd_data, "-----");
    end
end

initial begin
    #1000
    $fclose(fd_pc);
    $fclose(fd_data);
    $display("Files closed successfully.");
end

endmodule

```

```

module instruction_decoder(
    input [31:0] imem_insn,
    output reg [4:0] destination_reg,
    output reg [2:0] funct3,
    output reg [4:0] source_reg1,
    output reg [4:0] source_reg2,
    output reg [31:0] imm,           // 32-bit full immediate (after
// shift/sign-extension where needed)
    output reg [6:0] funct7,
    output reg [4:0] shamt,
    output reg [2:0] insn_type,     // 000: I-type, 001: R-type, 010:
// S-type, 011: Load,
// 100: U-type, 101: J-type, 110:
// Branch, 111: Default/NOP
    output reg alu_op_mux,
    output reg wen,
    output reg dmem_wen
);

always @ (*) begin
    case (imem_insn[6:0])
        // I-type instructions (e.g. ADDI, SLTI, ...)
        7'b0010011: begin
            insn_type      = 3'b000;
            destination_reg = imem_insn[11:7];
            funct3          = imem_insn[14:12];
            source_reg1     = imem_insn[19:15];
            source_reg2     = 5'b0;

```

```

    imm          = {{20{imem_insn[31]}}}, imem_insn[31:20]];
    funct7       = imem_insn[31:25];
    shamt        = imem_insn[24:20];
    alu_op_mux   = 1'b1;
    wen          = 1'b1;
    dmem_wen     = 1'b0;
end

// R-type instructions (e.g. ADD, SUB, ...)
7'b0110011: begin
    insn_type    = 3'b001;
    destination_reg = imem_insn[11:7];
    funct3       = imem_insn[14:12];
    source_reg1  = imem_insn[19:15];
    source_reg2  = imem_insn[24:20];
    funct7       = imem_insn[31:25];
    imm          = 32'b0;
    shamt        = 5'b0;
    alu_op_mux   = 1'b0;
    wen          = 1'b1;
    dmem_wen     = 1'b0;
end

// S-type instructions (Store instructions: e.g. SW)
7'b0100011: begin
    insn_type    = 3'b010;
    destination_reg = 5'b0;
    funct3       = imem_insn[14:12];
    source_reg1  = imem_insn[19:15];
    source_reg2  = imem_insn[24:20];
    // Construct immediate from imm[11:5] and imm[4:0].
    imm          = {{20{imem_insn[31]}}}, imem_insn[31:25],
imem_insn[11:7]];
    funct7       = 7'b0;
    shamt        = 5'b0;
    alu_op_mux   = 1'b1;
    wen          = 1'b0;
    dmem_wen     = 1'b1;
end

// Load instructions (e.g. LW)
7'b0000011: begin
    insn_type    = 3'b011;

```

```

    destination_reg = imem_insn[11:7];
    funct3          = imem_insn[14:12];
    source_reg1     = imem_insn[19:15];
    source_reg2     = 5'b0;
    imm             = {{20{imem_insn[31]}}}, imem_insn[31:20]];
    funct7          = 7'b0;
    shamt           = 5'b0;
    alu_op_mux      = 1'b1;
    wen             = 1'b1;
    dmem_wen        = 1'b0;
end

```

*// U-type instructions: LUI*

```

7'b0110111: begin
    insn_type       = 3'b100;
    destination_reg = imem_insn[11:7];
    funct3          = 3'b0; // not used
    source_reg1     = 5'b0;
    source_reg2     = 5'b0;
    // Immediate is bits [31:12] shifted left by 12.
    imm             = {imem_insn[31:12], 12'b0};
    funct7          = 7'b0;
    shamt           = 5'b0;
    alu_op_mux      = 1'b1;
    wen             = 1'b1;
    dmem_wen        = 1'b0;
end

```

*// U-type instructions: AUIPC*

```

7'b0010111: begin
    insn_type       = 3'b100;
    destination_reg = imem_insn[11:7];
    funct3          = 3'b0; // not used
    source_reg1     = 5'b0;
    source_reg2     = 5'b0;
    imm             = {imem_insn[31:12], 12'b0};
    funct7          = 7'b0;
    shamt           = 5'b0;
    alu_op_mux      = 1'b1;
    wen             = 1'b1;
    dmem_wen        = 1'b0;
end

```





```

        imem_insn[11:8], 1'b0};

    funct7      = 7'b0;
    shamt       = 5'b0;
    alu_op_mux  = 1'b0;
    wen         = 1'b0;
    dmem_wen    = 1'b0;
end

// Default case: Unknown instruction -> NOP.
default: begin
    insn_type    = 3'b111;
    destination_reg = 5'b0;
    funct3       = 3'b0;
    source_reg1  = 5'b0;
    source_reg2  = 5'b0;
    imm         = 32'b0;
    funct7       = 7'b0;
    shamt        = 5'b0;
    alu_op_mux   = 1'b0;
    wen          = 1'b1;
    dmem_wen     = 1'b0;
end
endcase
end
endmodule

```

```

module register_file(
    input clk,
    input rst_n,
    input wen,
    input [4:0] destination_reg,
    input [4:0] source_reg1,
    input [4:0] source_reg2,
    input [31:0] write_data,
    input [3:0] byte_en,
    output reg [31:0] read_data1,
    output reg [31:0] read_data2
);
    reg [31:0] registers [0:31];

    initial begin
        integer i;

```

```

        for (i = 0; i < 32; i = i + 1)
            registers[i] = 32'b0;
    end

    always @(*) begin
        read_data1 = registers[source_reg1];
        read_data2 = registers[source_reg2];
    end

    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            integer i;
            for (i = 0; i < 32; i = i + 1)
                registers[i] <= 32'b0;
        end else if (wen && (destination_reg != 5'b0)) begin
            //registers[destination_reg] <= write_data;
            if (byte_en[3])
                registers[destination_reg][31:24] <= #0.1
write_data[31:24];
            if (byte_en[2])
                registers[destination_reg][23:16] <= #0.1
write_data[23:16];
            if (byte_en[1])
                registers[destination_reg][15:8] <= #0.1
write_data[15:8];
            if (byte_en[0])
                registers[destination_reg][7:0] <= #0.1
write_data[7:0];
        end
    end
endmodule

```

### Code Explanation:


In this lab, we are going to be adding branch instructions into our project. These branch instructions are processed by being identified during the decode stage, where both operands and immediate offsets are extracted. The branch is based on operand and the funct3 is made in the execute stage only if the condition is met. Then, the program counter is updated to the branch target address. Finally, the pipeline flushes the next instruction when fetched and stalls when new instructions are loaded.

The way our flush logic works is that we trigger a flush flag as soon as the EX stage result confirms we will be jumping, at which point we spend the next clock cycle stalling to load the instruction at the jump address. After this point, the CPU continues as normal. One important part of the flush that we had to account for is the event in which two jump instructions


enter the pipeline. It's important that we ignore the jump signal from the latter instruction preemptively, as if it reaches our execution logic then it will override the first jump. To do so, we have combinational wires in place to ensure that we only jump to a new address under valid conditions, for example when our pipeline is not actively being flushed.

Aside from flush logic, the top-level of our CPU is mostly the same, albeit cleaned and organized from top to bottom since lab 6. The major module changes are in the PC, Decoder, and ALU which all have to accommodate for the new instructions. We also made some changes to our write logic in the regfile, not out of necessity for the lab but for ease of debugging, such that the write-enable flag is no longer just a flag, but a bus indicating which bits of the register must be overwritten.

### Waveforms:

 

Values in registers 5, 6, 7.

 

Values in register 28, 29, 30, 31

## Trace Files:

### PC Counter Trace File

3	PC: 0x00000004
4	PC: 0x00000008
5	PC: 0x0000000c
6	PC: 0x00000010
7	PC: 0x00000014
8	PC: 0x00000018
9	PC: 0x0000001c
10	PC: 0x00000020
11	PC: 0x00000024
12	PC: 0x00000028
13	PC: 0x0000002c
14	PC: 0x00000030
15	PC: 0x00000034
16	PC: 0x00000000
17	PC: 0x00000038
18	PC: 0x0000003c
19	PC: 0x00000000
20	PC: 0x00000044
21	PC: 0x00000048
22	PC: 0x0000004c
23	PC: 0x00000050
24	PC: 0x00000054
25	PC: 0x00000058
26	PC: 0x00000000
27	PC: 0x00000048
28	PC: 0x0000004c
29	PC: 0x00000050
30	PC: 0x00000054
31	PC: 0x00000058
32	PC: 0x00000000
33	PC: 0x00000048
34	PC: 0x0000004c
35	PC: 0x00000050
36	PC: 0x00000054
37	PC: 0x00000058
38	PC: 0x00000000
39	PC: 0x00000048
40	PC: 0x0000004c
41	PC: 0x00000000
42	PC: 0x00000058
43	PC: 0x0000005c
44	PC: 0x00000060
45	PC: 0x00000064
46	PC: 0x00000068
47	PC: 0x0000006c
48	PC: 0x00000070
49	

## MEM WB result and destination trace file

```
12 -----
13 MEM_WB_result: 268500992
14 MEM_WB_dest: 5
15 -----
16 MEM_WB_result: 268500992
17 MEM_WB_dest: 5
18 -----
19 MEM_WB_result: -3
20 MEM_WB_dest: 6
21 -----
22 MEM_WB_result: 268500992
23 MEM_WB_dest: 5
24 -----
25 MEM_WB_result: 268500996
26 MEM_WB_dest: 5
27 -----
28 MEM_WB_result: 7
29 MEM_WB_dest: 7
30 -----
31 MEM_WB_result: 268500992
32 MEM_WB_dest: 5
33 -----
34 MEM_WB_result: 268501000
35 MEM_WB_dest: 5
36 -----
37 MEM_WB_result: 25
38 MEM_WB_dest: 28
39 -----
40 MEM_WB_result: 0
41 MEM_WB_dest: 29
42 -----
43 MEM_WB_result: -3
44 MEM_WB_dest: 0
45 -----
46 MEM_WB_result: 3
47 MEM_WB_dest: 30
48 -----
49 MEM_WB_result: 0
50 MEM_WB_dest: 0
51 -----
52 MEM_WB_result: 0
53 MEM_WB_dest: 0
54 -----
55 MEM_WB_result: 0
56 MEM_WB_dest: 0
57 -----
58 MEM_WB_result: 0
59 MEM_WB_dest: 0
60 -----
61 MEM_WB_result: 0
62 MEM_WB_dest: 0
63 -----
64 MEM_WB_result: 0
65 MEM_WB_dest: 0
66 -----
67 MEM_WB_result: 7
68 MEM_WB_dest: 31
69 -----
70 MEM_WB_result: 3
71 MEM_WB_dest: 0
```

```

71 MEM_WB_dest: 0
72 -----
73 MEM_WB_result: 7
74 MEM_WB_dest: 29
75 -----
76 MEM_WB_result: 2
77 MEM_WB_dest: 30
78 -----
79 MEM_WB_result: 0
80 MEM_WB_dest: 0
81 -----
82 MEM_WB_result: 0
83 MEM_WB_dest: 0
84 -----
85 MEM_WB_result: 0
86 MEM_WB_dest: 0
87 -----
88 MEM_WB_result: 2
89 MEM_WB_dest: 0
90 -----
91 MEM_WB_result: 14
92 MEM_WB_dest: 29
93 -----
94 MEM_WB_result: 1
95 MEM_WB_dest: 30
96 -----
97 MEM_WB_result: 0
98 MEM_WB_dest: 0
99 -----
100 MEM_WB_result: 0
101 MEM_WB_dest: 0
102 -----
103 MEM_WB_result: 0
104 MEM_WB_dest: 0
105 -----
106 MEM_WB_result: 1
107 MEM_WB_dest: 0
108 -----
109 MEM_WB_result: 21
110 MEM_WB_dest: 29
111 -----
112 MEM_WB_result: 0
113 MEM_WB_dest: 30
114 -----
115 MEM_WB_result: 0
116 MEM_WB_dest: 0
117 -----
118 MEM_WB_result: 0
119 MEM_WB_dest: 0
120 -----
121 MEM_WB_result: 0
122 MEM_WB_dest: 0
123 -----
124 MEM_WB_result: 0
125 MEM_WB_dest: 0
126 -----
127 MEM_WB_result: 0
128 MEM_WB_dest: 0
129 -----
130 MEM_WB_result: 0
131 MEM_WB_dest: 0
132 -----
133 MEM_WB_result: -6
134 MEM_WB_dest: 5
135 -----
136 MEM_WB_result: -6
137 MEM_WB_dest: 0
138 -----
139 MEM_WB_result: -21
140 MEM_WB_dest: 29
141 -----
142 MEM_WB_result: 4
143 MEM_WB_dest: 29
144 -----
145

```

**Lab Learnings:**

This lab builds on top of the stuff from Labs 4, 5, and 6. This lab implements the jump and branch instructions. The branch is already known at the decode stage and the next instruction has been fetched so the pipeline has to flush the fetched instruction and then stall until the branch is resolved. Then the branch is resolved at the end of the execution stage, then the stall ends and the next instruction is fetched from the branch target.